

ELEC 361 Measurement and Analysis


Lab 2. Time and frequency response of RC circuits

References

- Theoretical & Computer Analysis of Systems & Networks - Bold and Tan (text for ELEC 353)
- The Art of Electronics - Horowitz and Hill, section 1.13, 1.14, 1.19
- Signals and Systems - H. P. Hsu, section 5.47 (on Bode plots)

Pre-lab homework

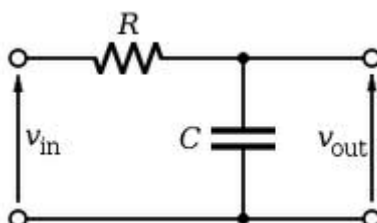1. Read the following:
 - The Art of Electronics - Horowitz and Hill, section 1.13, 1.14, 1.19
 - Signals and Systems - H. P. Hsu, section 5.47 (on Bode plots)
2. For the following RC circuit




- i. Use simple arguments about the components to determine the behaviour of this circuit for sinusoidal signals at very high frequency, and at d.c.
 - ii. The step response is the output voltage when the input voltage steps from 0 V to 1 V instantaneously at time $t=0$. Use simple arguments about the components to determine the step-response of this circuit at times immediately after $t=0$, and after a long time.
3. Calculate the time constant of the circuit, and explain how it relates to the corner frequency (also called the '3dB point') for the circuit.
 4. Can you justify the reasons for this circuit being called a 'low pass filter' and a 'quasi integrator'?
 5. What is the time constant of the circuit when a second resistor of value R is put in parallel with the capacitor?


Lab tasks

Task 1: For each of the following RC filters:


1. Simple low-pass

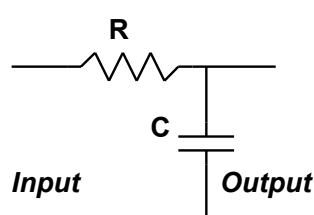


2. "Quasi Differentiator"

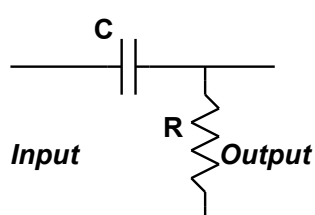

3. Lossy low-pass

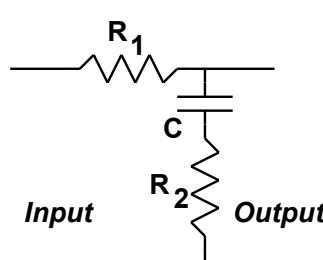

4. Lossy High Pass

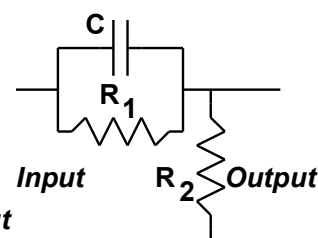

Build the circuit with some sensible component values, and then use the NI ELVIS II

